

Quiz Assignment 4

(Deadline : 4th, October 2020)

Instructions

- The quiz contains 10 questions, for a total of 20 points.
- The score for each question is given next to each question, there are no negative marks.
- Each question has only one correct choice, unless specified otherwise.
- All qubit states/operations are given in the big endian notation.

Questions

1. It is always possible to copy the state of one qubit into another qubit. [**1 point**]
a) True b) False
2. A quantum gate is a physical object and the qubit state changes when it interacts with this object. [**1 point**]
a) True b) False
3. A classical computer is required in order to use a quantum computer. [**1 point**]
a) True b) False

4. The quantum oracle of an n -bit Boolean function requires a quantum computer with exactly n -qubits. [1 point]

a) True b) False

5. The operation performed on the two-qubit system in the quantum circuit shown in (Figure 1) is: [2 points]

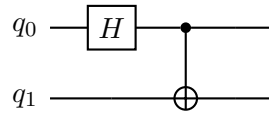


Figure 1: Circuit for Question 5

- a) $(H \otimes I) \circ \text{CNOT}$ b) $(H \otimes H) \circ \text{CNOT}$
 c) $\text{CNOT} \circ (H \otimes I)$ d) $\text{CNOT} \circ (I \otimes H)$

6. The operation performed on the two-qubit system in the quantum circuit shown in (Figure 2) is: [2 points]

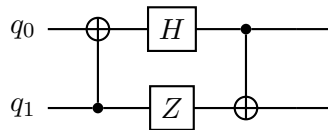


Figure 2: Circuit for Question 6

- a) $\text{CNOT}_0^1 \circ (H \otimes Z) \circ \text{CNOT}_0^1$ b) $\text{CNOT}_1^0 \circ (H \otimes Z) \circ \text{CNOT}_0^1$
 c) $\text{CNOT}_0^1 \circ (H \otimes Z) \circ \text{CNOT}_1^0$ d) $\text{CNOT}_1^0 \circ (H \otimes Z)$

7. The operation performed by the gates in the shaded area of the quantum circuit in (Figure 3) is: [**1 points**]

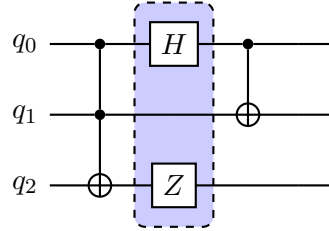


Figure 3: Circuit for Question 7

- | | |
|------------------------------|------------------------------|
| a) $(Z \otimes I \otimes H)$ | b) $(H \otimes Z)$ |
| c) $(H \otimes I \otimes Z)$ | d) $(H \otimes Z \otimes I)$ |

8. The resultant state for the quantum circuit shown in (Figure 4) is: [**3 points**]

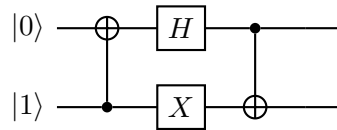


Figure 4: Circuit for Question 8

- | | |
|---|---|
| a) $\frac{1}{\sqrt{2}} (00\rangle + 11\rangle)$ | b) $\frac{1}{\sqrt{2}} (00\rangle - 11\rangle)$ |
| c) $\frac{1}{\sqrt{2}} (00\rangle - 01\rangle)$ | d) $\frac{1}{\sqrt{2}} (00\rangle - 10\rangle)$ |

9. The resultant state for the quantum circuit shown in (Figure 5) is: [4 points]

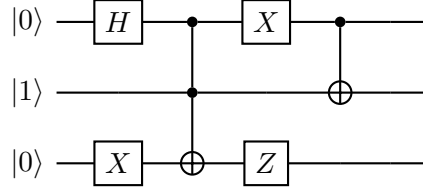


Figure 5: Circuit for Question 9

- a) $\frac{1}{\sqrt{2}} (|000\rangle - |111\rangle)$ b) $\frac{1}{\sqrt{2}} (|010\rangle - |101\rangle)$
c) $\frac{1}{\sqrt{2}} (|011\rangle - |101\rangle)$ d) $\frac{1}{\sqrt{2}} (|100\rangle - |111\rangle)$
10. The Boolean function represented by the oracle given in (Figure 6), where $x_0, x_1 \in \{0, 1\}$ and $+$ denotes the XOR operation. More than one option may be correct: [4 points]

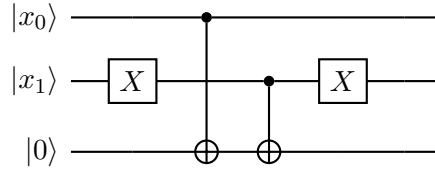


Figure 6: Circuit for Question 10

- a) $x_0 + \overline{x_1}$ b) $\overline{x_0 + x_1}$
c) $\overline{x_0} + \overline{x_1}$ d) $1 + x_0 + x_1$